

THREE PHASE VOLTAGE SOURCE INVERTER

Circuit Done By:- K.Mohamed Abdullah


Department of EEE,

St.Xaviers Catholic College of Engineering,nagercoil

Theory:-

In this a 3-phase bridge type VSI with square wave pole voltages has been considered. The output from this inverter is to be fed to a 3-phase balanced load. This circuit may be identified as three single-phase half-bridge inverter circuits put across the same dc bus. The individual pole voltages of the 3-phase bridge circuit are identical to the square pole voltages output by single-phase half bridge or full bridge circuits. The three pole voltages of the 3-phase square wave inverter are shifted in time by one third of the output time period. the phase sequence of the pole voltages is taken as V_{AO} , V_{BO} and V_{CO} . The numbering of the switches in Fig. has some special significance vis-à-vis the output phase sequence.

CIRCUIT DIAGRAM:-

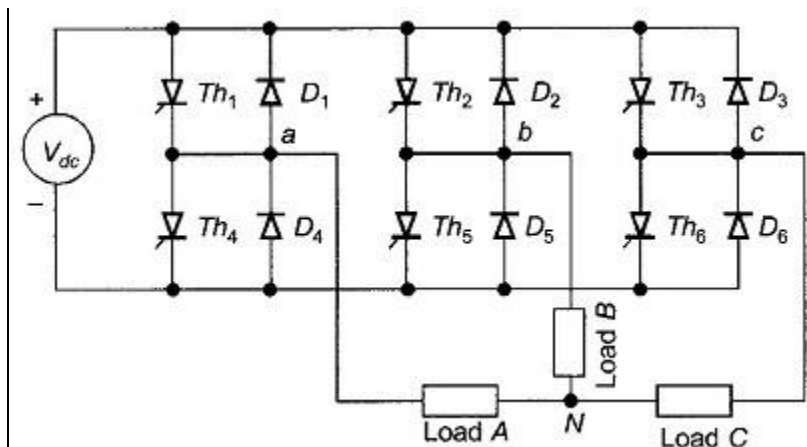

Schematic Diagram: the circuit schematic of the three phase voltage source inverter in eSim is as shown below

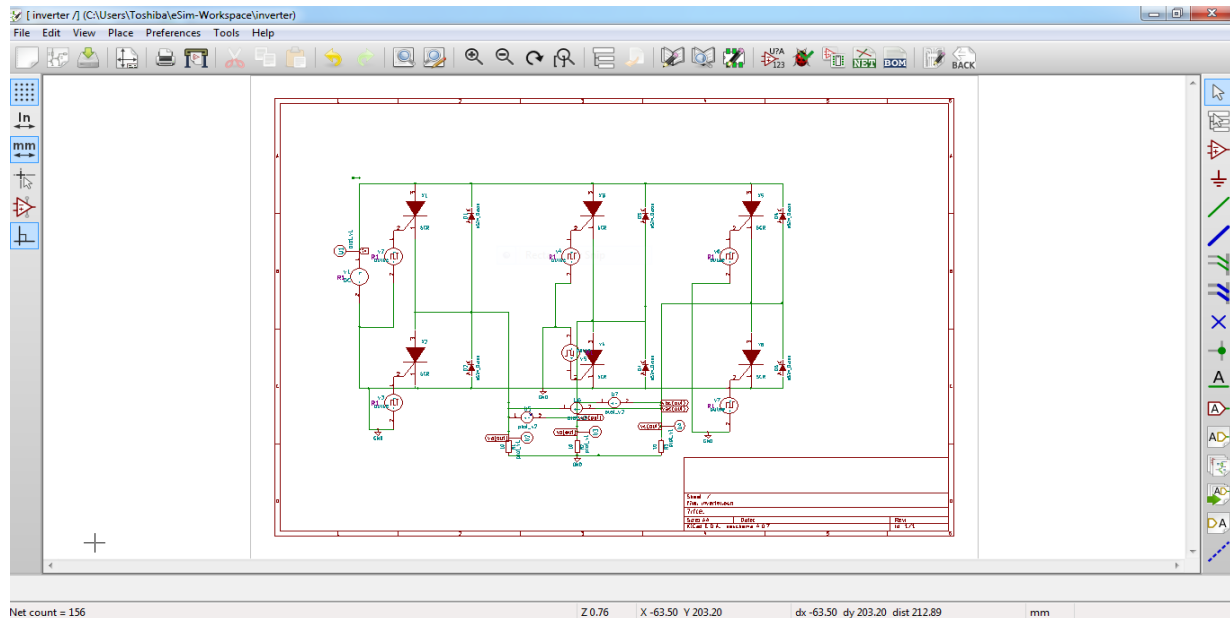


Figure 1:three phase voltage source inverter

Simulation Results:-

1. Ngspice Plots

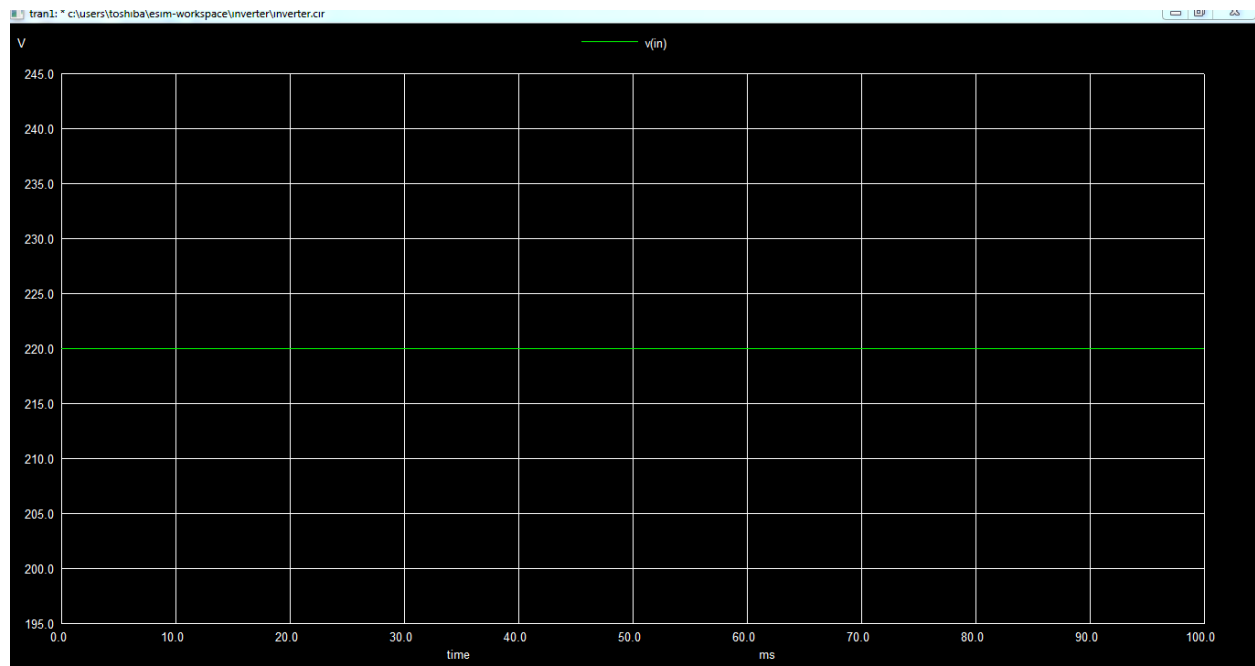


Figure 2:- input dc voltage

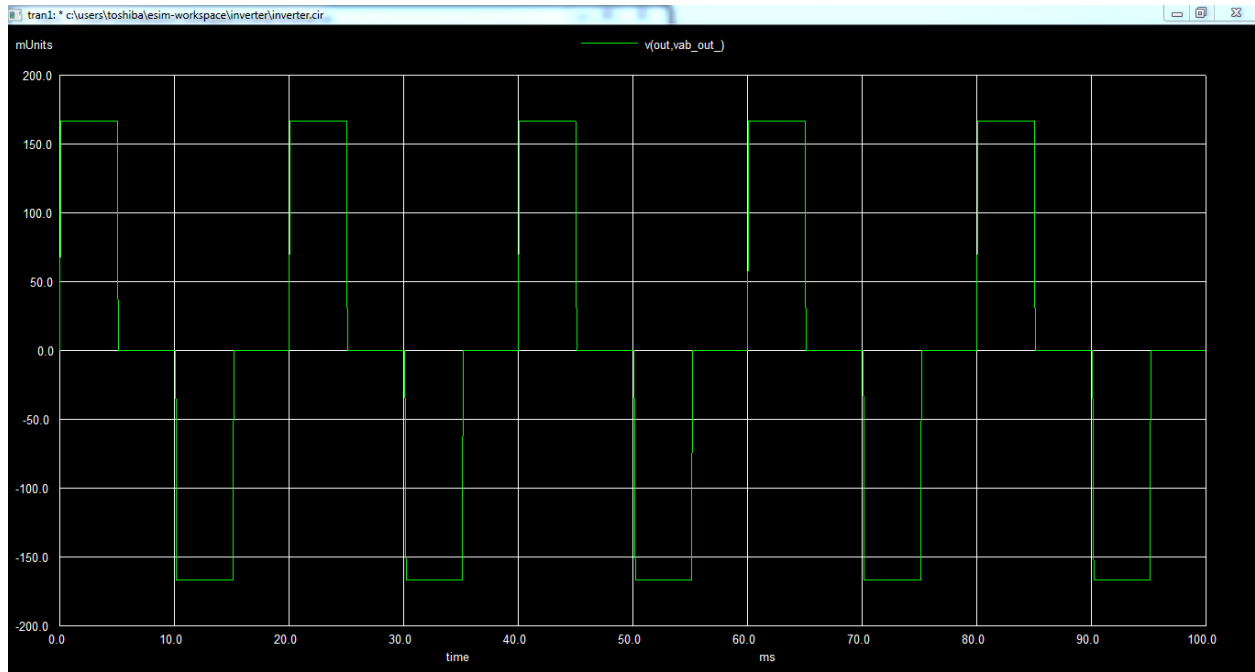


Figure 3:- Output voltage of Vab

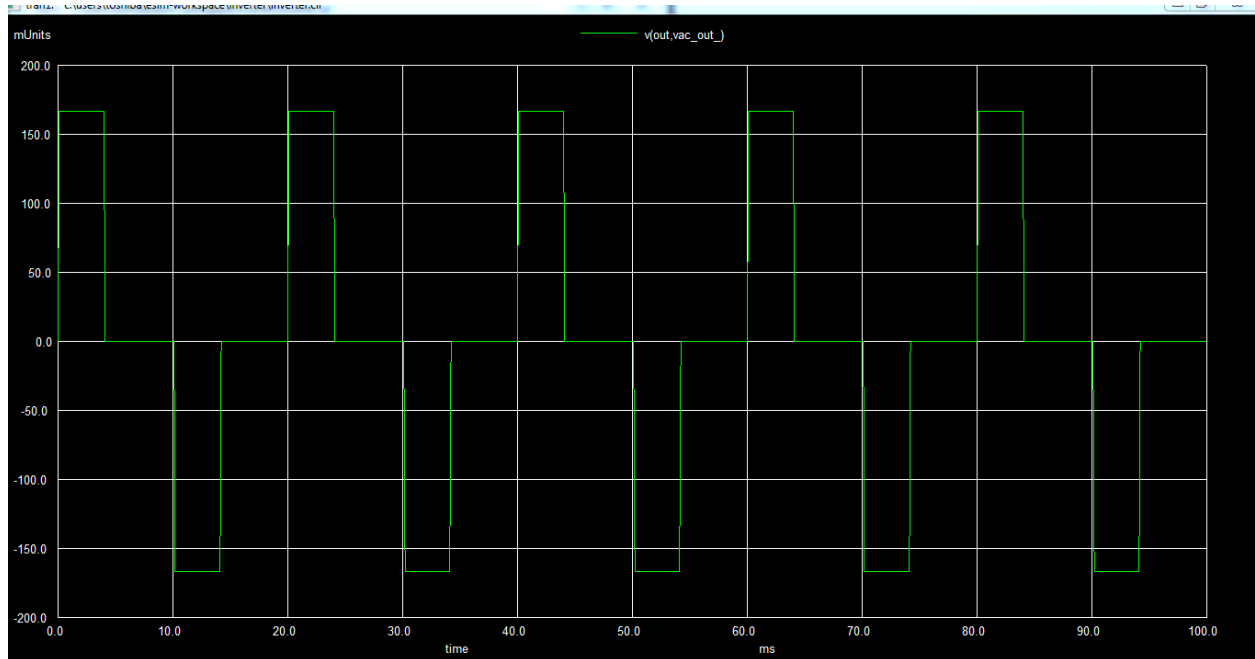


Figure 4:- Output voltage of Vac

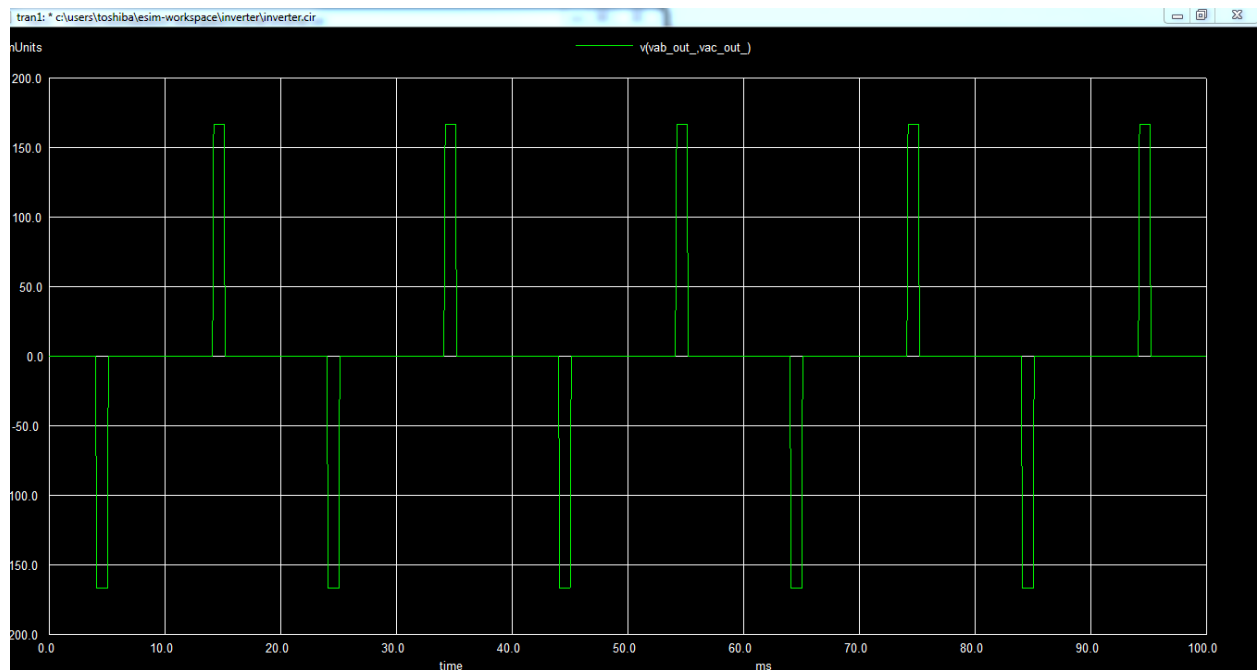


Figure 5:- Output vottage of Vbc

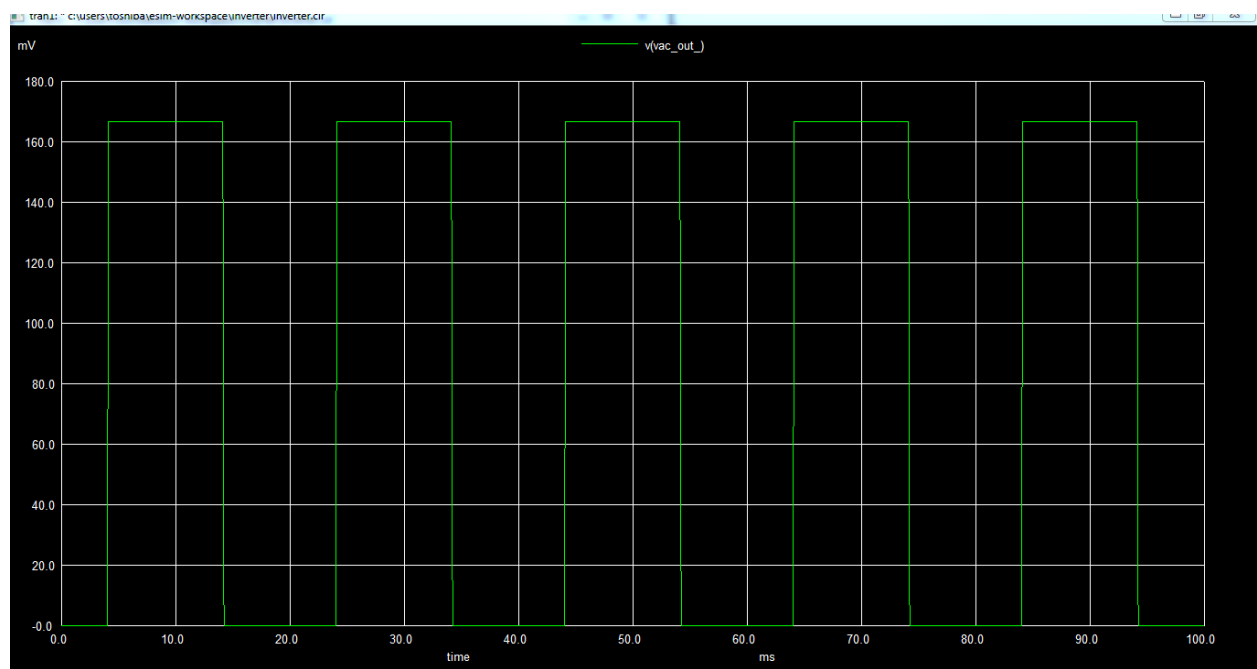


Figure 6:-Output voltage of Va

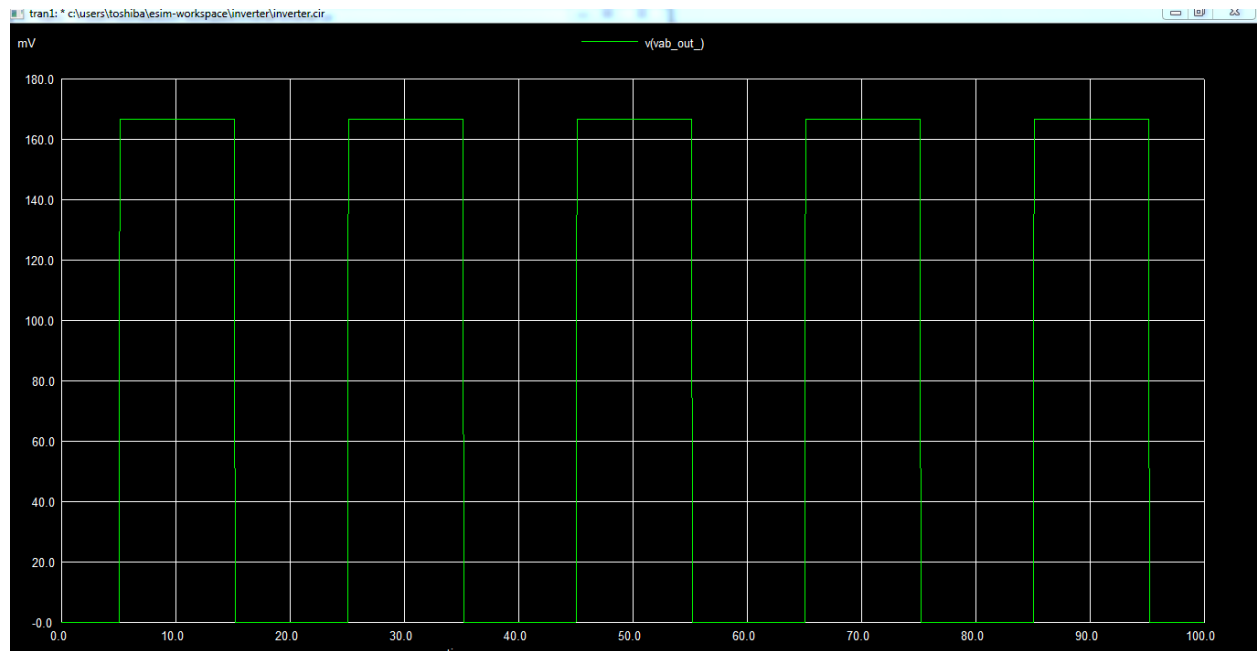


Figure 7:-Output voltage of Vb

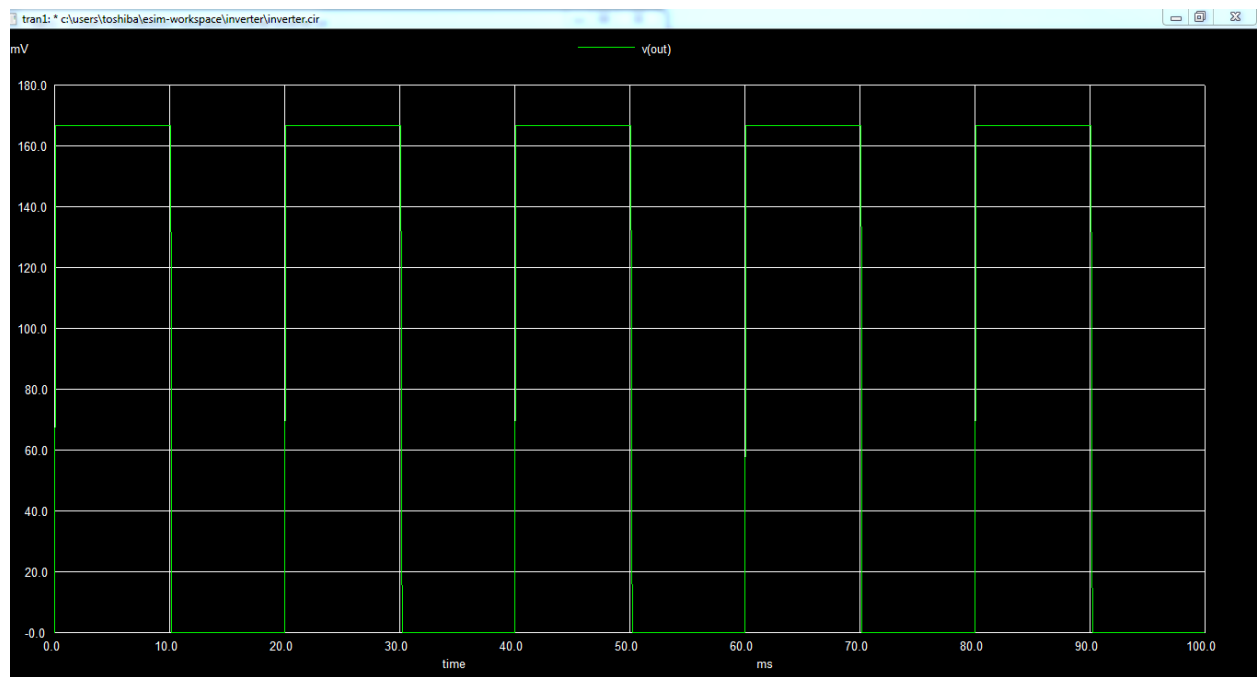


Figure 8:- Output voltage of Vc

2. Python Plots:

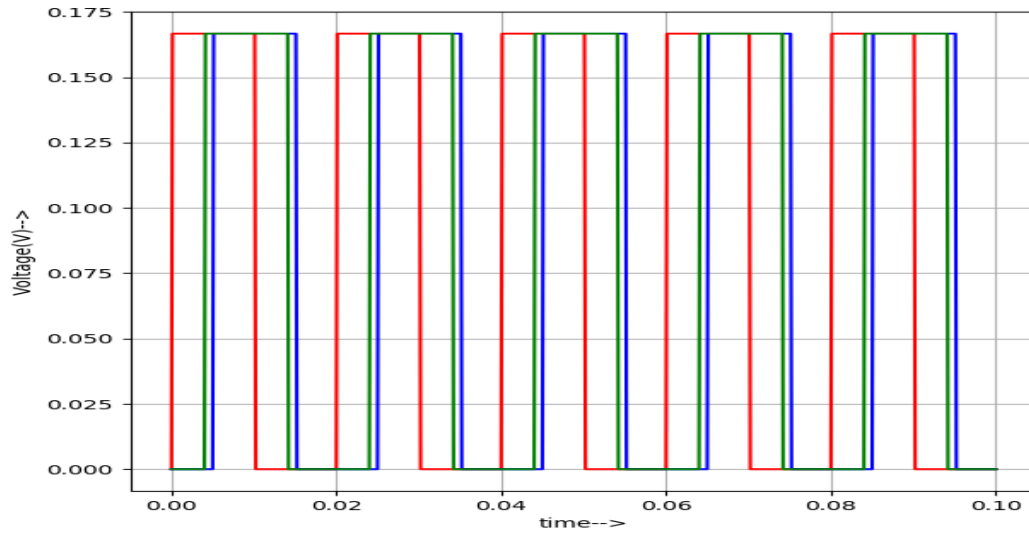


Figure 9:- python plot of combined Va,Vb,Vc vs time

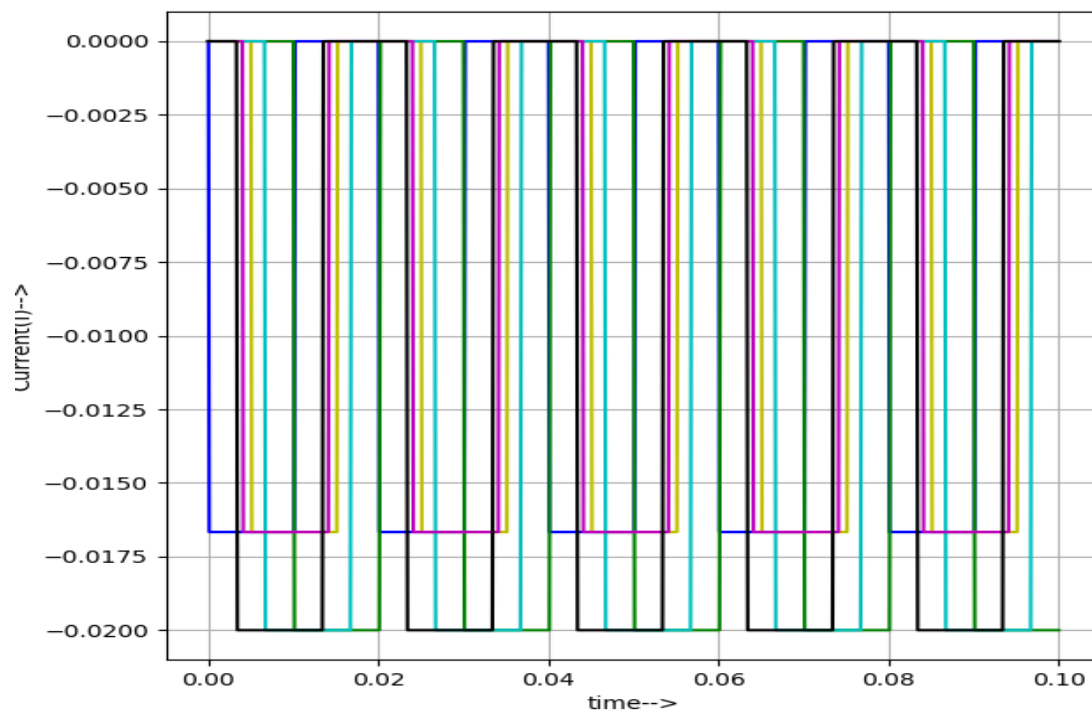


Figure 10:-python plot of combined Iab,Ibc,Ica vs time

References :

<https://www.sciencedirect.com/science/article/pii/B9780128117989000068>