


TITLE OF THE EXPERIMENT -

4 BIT SYNCHRONOUS SERIAL IN SERIAL OUT SHIFT REGISTER

Abstract:

Shift Register is a group of flip flops used to store / move multiple bits of data. In Serial-in to Serial-out (SISO) shift register the data is shifted serially “IN” and “OUT” of the register, one bit at a time in either a left or right direction under clock control. It allows serial input i.e. one bit after the other through a single data line and produces a serial output. There is only one output, the data leaves the shift register one bit at a time in a serial pattern. The circuit consists of four D flip-flops which are connected in a serial manner. All these flip-flops are synchronous with each other since the same clock signal is applied to each flip flop.


Circuit Diagram:

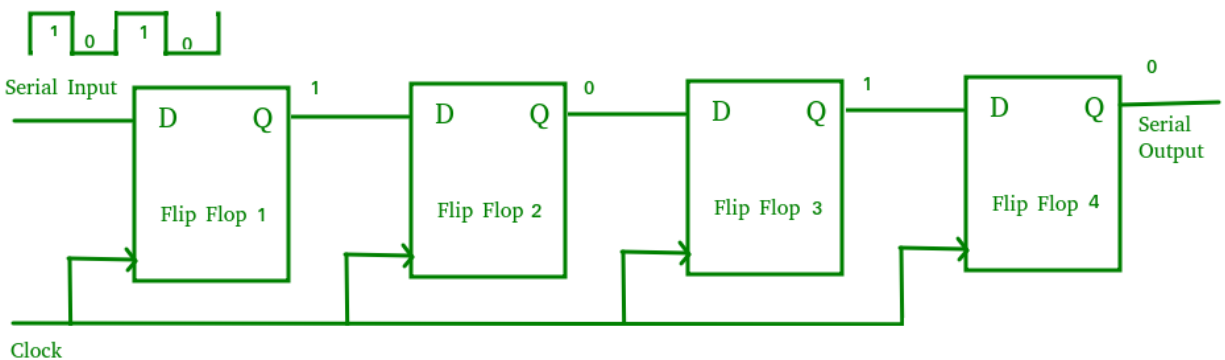

Truth Table:

Operation of the Shift-right Register					
Timing pulse	Q_A	Q_B	Q_C	Q_D	Serial output at Q_D
Initial value	0	0	0	0	0
After 1 st clock pulse	1	0	0	0	0
After 2 nd clock pulse	1	1	0	0	0
After 3 rd clock pulse	0	1	1	0	0
After 4 th clock pulse	1	0	1	1	1


Timing Diagram:

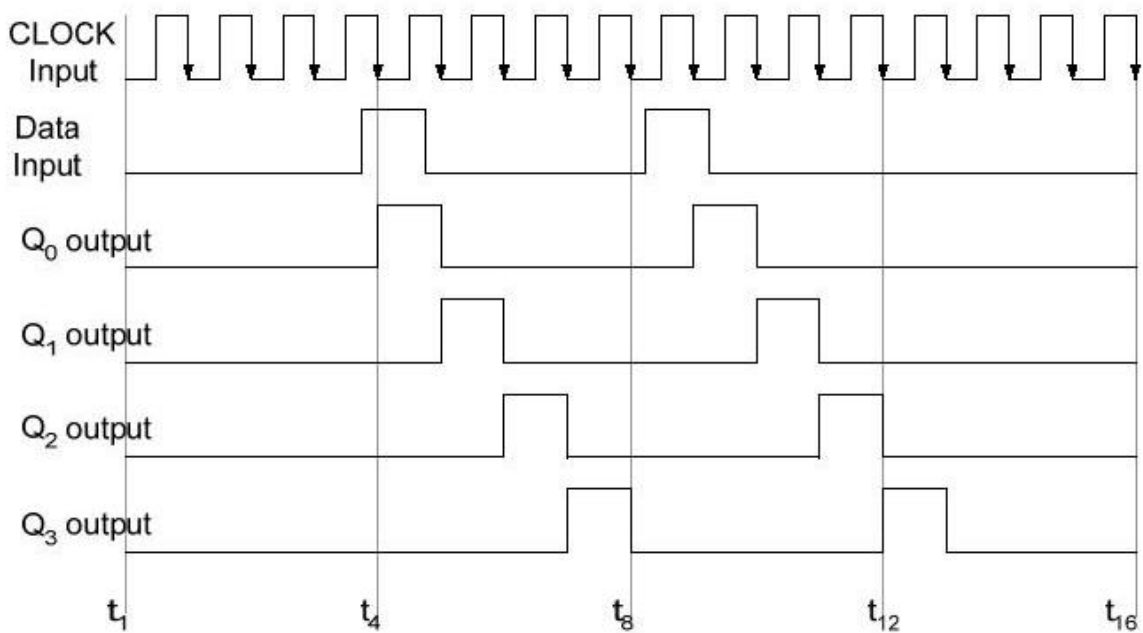


eSim Required Components :



Synchronous up counter	
Component Name	Type
d_dff	d flip flop
clock	clock input
DC	dc voltage source for logic 1

ESIM Circuit design snapshot:

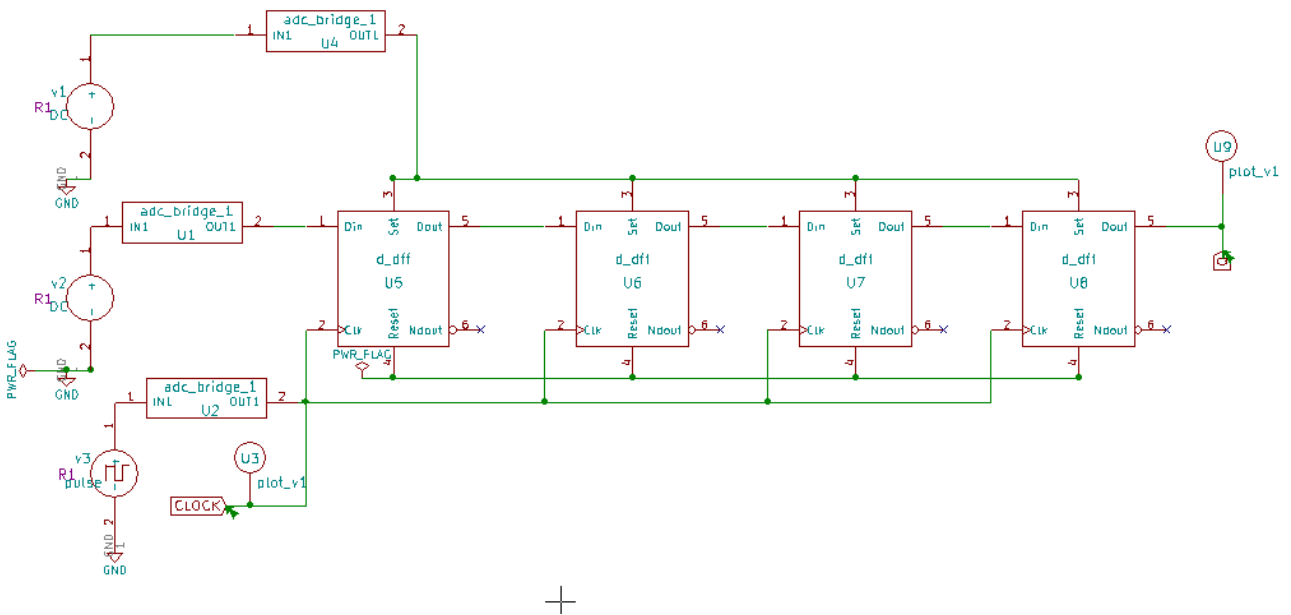

OUTPUT –

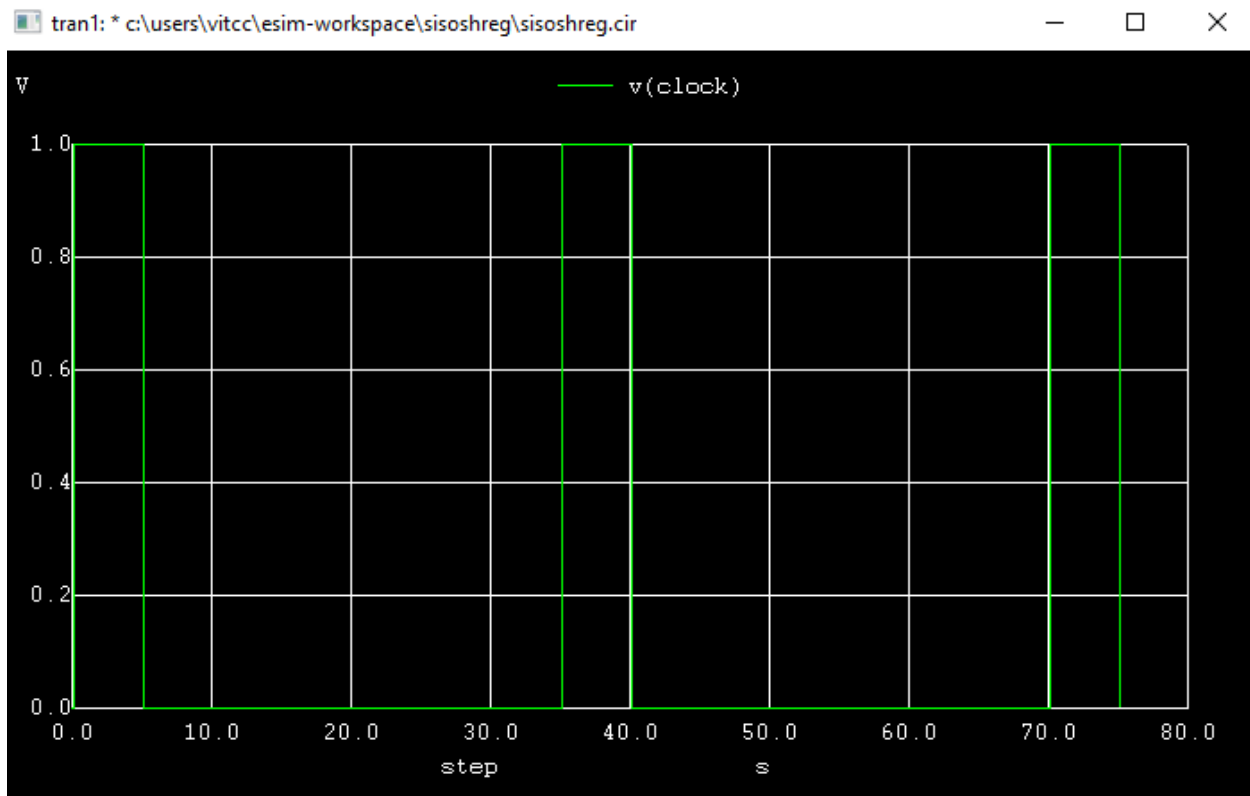

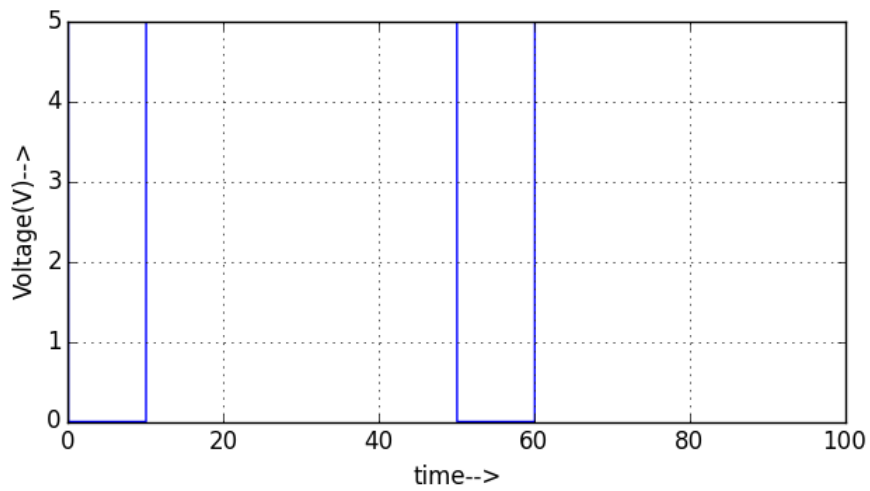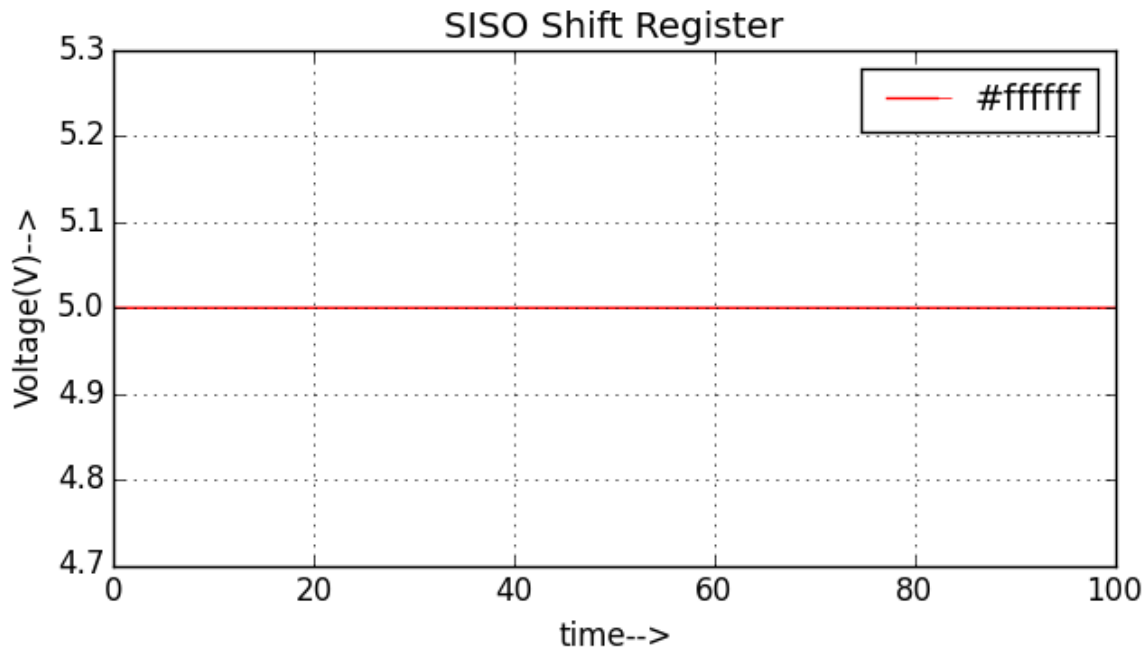

References:

- <https://www.electrical4u.com/serial-in-serial-out-siso-shift-register/>
- <https://www.geeksforgeeks.org/shift-registers-in-digital-logic/>